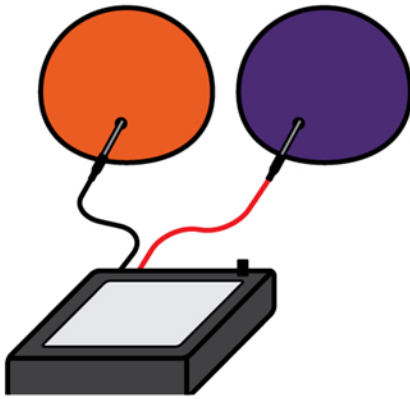


## Let's investigate a simple circuit using Squishy Circuits.


- 1** Take two pieces of conductive dough and put each battery terminal into one of the pieces.




- 2** Find a LED and separate the terminals apart. Notice one is longer than the other.



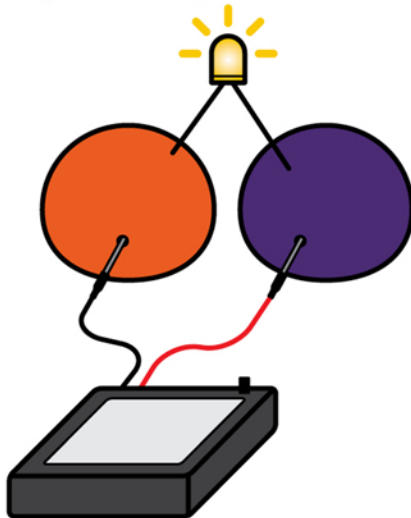
- 3** Create a circuit by placing each terminal of the LED in the conductive dough pieces. The longer LED terminal should go in the dough with the red battery pack wire.



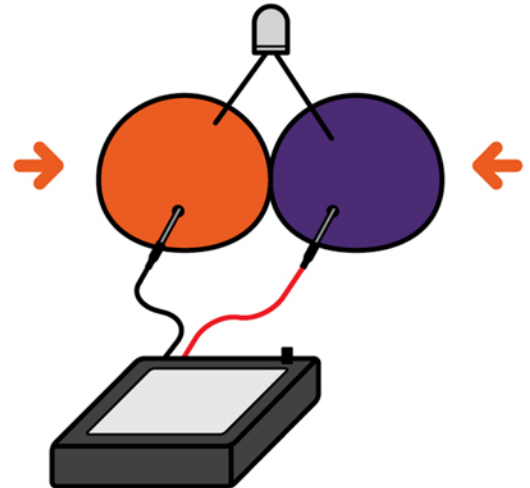- 4** Try making a short circuit by pushing the dough pieces together. Notice the LED dims or goes out.



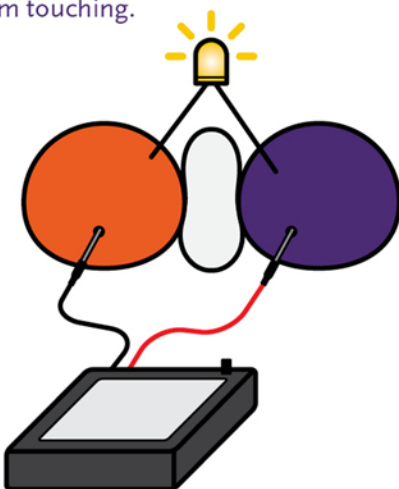- 5** Optional: To prevent short circuits, use the insulating dough to keep the conductive dough from touching.



- 6** Get creative! Try using motors, buzzers, and more LEDs for your creations!

